

Chapter 27

1. (a) Let i be the current in the circuit and take it to be positive if it is to the left in R_1 . We use Kirchhoff's loop rule: $\varepsilon_1 - iR_2 - iR_1 - \varepsilon_2 = 0$. We solve for i :

$$i = \frac{\varepsilon_1 - \varepsilon_2}{R_1 + R_2} = \frac{12 \text{ V} - 6.0 \text{ V}}{4.0 \Omega + 8.0 \Omega} = 0.50 \text{ A}.$$

A positive value is obtained, so the current is counterclockwise around the circuit.

If i is the current in a resistor R , then the power dissipated by that resistor is given by $P = i^2 R$.

(b) For R_1 , $P_1 = i^2 R_1 = (0.50 \text{ A})^2 (4.0 \Omega) = 1.0 \text{ W}$,

(c) and for R_2 , $P_2 = i^2 R_2 = (0.50 \text{ A})^2 (8.0 \Omega) = 2.0 \text{ W}$.

If i is the current in a battery with emf ε , then the battery supplies energy at the rate $P = i\varepsilon$ provided the current and emf are in the same direction. The battery absorbs energy at the rate $P = i\varepsilon$ if the current and emf are in opposite directions.

(d) For ε_1 , $P_1 = i\varepsilon_1 = (0.50 \text{ A})(12 \text{ V}) = 6.0 \text{ W}$

(e) and for ε_2 , $P_2 = i\varepsilon_2 = (0.50 \text{ A})(6.0 \text{ V}) = 3.0 \text{ W}$.

(f) In battery 1 the current is in the same direction as the emf. Therefore, this battery supplies energy to the circuit; the battery is discharging.

(g) The current in battery 2 is opposite the direction of the emf, so this battery absorbs energy from the circuit. It is charging.

5. The chemical energy of the battery is reduced by $\Delta E = q\varepsilon$, where q is the charge that passes through in time $\Delta t = 6.0 \text{ min}$, and ε is the emf of the battery. If i is the current, then $q = i \Delta t$ and

$$\Delta E = i\varepsilon \Delta t = (5.0 \text{ A})(6.0 \text{ V})(6.0 \text{ min})(60 \text{ s/min}) = 1.1 \times 10^4 \text{ J}.$$

We note the conversion of time from minutes to seconds.

6. (a) The cost is $(100 \text{ W} \cdot 8.0 \text{ h} / 2.0 \text{ W} \cdot \text{h})(\$0.80) = \$3.2 \times 10^2$.

(b) The cost is $(100 \text{ W} \cdot 8.0 \text{ h}/10^3 \text{ W} \cdot \text{h}) (\$0.06) = \$0.048 = 4.8 \text{ cents}$.

7. (a) The energy transferred is

$$U = Pt = \frac{\varepsilon^2 t}{r + R} = \frac{(2.0 \text{ V})^2 (2.0 \text{ min}) (60 \text{ s/min})}{1.0 \Omega + 5.0 \Omega} = 80 \text{ J}.$$

(b) The amount of thermal energy generated is

$$U' = i^2 R t = \left(\frac{\varepsilon}{r + R} \right)^2 R t = \left(\frac{2.0 \text{ V}}{1.0 \Omega + 5.0 \Omega} \right)^2 (5.0 \Omega) (2.0 \text{ min}) (60 \text{ s/min}) = 67 \text{ J}.$$

(c) The difference between U and U' , which is equal to 13 J, is the thermal energy that is generated in the battery due to its internal resistance.

10. (a) We solve $i = (\varepsilon_2 - \varepsilon_1)/(r_1 + r_2 + R)$ for R :

$$R = \frac{\varepsilon_2 - \varepsilon_1}{i} - r_1 - r_2 = \frac{3.0 \text{ V} - 2.0 \text{ V}}{1.0 \times 10^{-3} \text{ A}} - 3.0 \Omega - 3.0 \Omega = 9.9 \times 10^2 \Omega.$$

(b) $P = i^2 R = (1.0 \times 10^{-3} \text{ A})^2 (9.9 \times 10^2 \Omega) = 9.9 \times 10^{-4} \text{ W}$.

15. Let the emf be V . Then $V = iR = i'(R + R')$, where $i = 5.0 \text{ A}$, $i' = 4.0 \text{ A}$, and $R' = 2.0 \Omega$. We solve for R :

$$R = \frac{i'R'}{i - i'} = \frac{(4.0 \text{ A})(2.0 \Omega)}{5.0 \text{ A} - 4.0 \text{ A}} = 8.0 \Omega.$$

18. The currents i_1 , i_2 and i_3 are obtained from Eqs. 27-18 through 27-20:

$$i_1 = \frac{\varepsilon_1(R_2 + R_3) - \varepsilon_2 R_3}{R_1 R_2 + R_2 R_3 + R_1 R_3} = \frac{(4.0 \text{ V})(10 \Omega + 5.0 \Omega) - (1.0 \text{ V})(5.0 \Omega)}{(10 \Omega)(10 \Omega) + (10 \Omega)(5.0 \Omega) + (10 \Omega)(5.0 \Omega)} = 0.275 \text{ A},$$

$$i_2 = \frac{\varepsilon_1 R_3 - \varepsilon_2(R_1 + R_2)}{R_1 R_2 + R_2 R_3 + R_1 R_3} = \frac{(4.0 \text{ V})(5.0 \Omega) - (1.0 \text{ V})(10 \Omega + 5.0 \Omega)}{(10 \Omega)(10 \Omega) + (10 \Omega)(5.0 \Omega) + (10 \Omega)(5.0 \Omega)} = 0.025 \text{ A},$$

$$i_3 = i_2 - i_1 = 0.025 \text{ A} - 0.275 \text{ A} = -0.250 \text{ A}.$$

$V_d - V_c$ can now be calculated by taking various paths. Two examples: from $V_d - i_2 R_2 = V_c$ we get

$$V_d - V_c = i_2 R_2 = (0.0250 \text{ A})(10 \Omega) = +0.25 \text{ V};$$

from $V_d + i_3 R_3 + \mathcal{E}_2 = V_c$ we get

$$V_d - V_c = i_3 R_3 - \mathcal{E}_2 = -(-0.250 \text{ A})(5.0 \Omega) - 1.0 \text{ V} = +0.25 \text{ V}.$$

22. (a) $R_{\text{eq}}(FH) = (10.0 \Omega)(10.0 \Omega)(5.00 \Omega)/[(10.0 \Omega)(10.0 \Omega) + 2(10.0 \Omega)(5.00 \Omega)] = 2.50 \Omega$.

(b) $R_{\text{eq}}(FG) = (5.00 \Omega) R/(R + 5.00 \Omega)$, where

$$R = 5.00 \Omega + (5.00 \Omega)(10.0 \Omega)/(5.00 \Omega + 10.0 \Omega) = 8.33 \Omega.$$

So $R_{\text{eq}}(FG) = (5.00 \Omega)(8.33 \Omega)/(5.00 \Omega + 8.33 \Omega) = 3.13 \Omega$.

26. The part of R_0 connected in parallel with R is given by $R_1 = R_0 x/L$, where $L = 10 \text{ cm}$. The voltage difference across R is then $V_R = \mathcal{E}R'/R_{\text{eq}}$, where $R' = RR_1/(R + R_1)$ and

$$R_{\text{eq}} = R_0(1 - x/L) + R'.$$

Thus,

$$P_R = \frac{V_R^2}{R} = \frac{1}{R} \left(\frac{\mathcal{E}RR_1/(R + R_1)}{R_0(1 - x/L) + RR_1/(R + R_1)} \right)^2 = \frac{100R(\mathcal{E}x/R_0)^2}{(100R/R_0 + 10x - x^2)^2},$$

where x is measured in cm.

64. (a) The potential difference V across the plates of a capacitor is related to the charge q on the positive plate by $V = q/C$, where C is capacitance. Since the charge on a discharging capacitor is given by $q = q_0 e^{-t/\tau}$, this means $V = V_0 e^{-t/\tau}$ where V_0 is the initial potential difference. We solve for the time constant τ by dividing by V_0 and taking the natural logarithm:

$$\tau = -\frac{t}{\ln(V/V_0)} = -\frac{10.0 \text{ s}}{\ln[(1.00 \text{ V})/(100 \text{ V})]} = 2.17 \text{ s}.$$

(b) At $t = 17.0 \text{ s}$, $t/\tau = (17.0 \text{ s})/(2.17 \text{ s}) = 7.83$, so

$$V = V_0 e^{-t/\tau} = (100 \text{ V})e^{-7.83} = 3.96 \times 10^{-2} \text{ V}.$$