

Chapter 31

9. The time required is $t = T/4$, where the period is given by $T = 2\pi/\omega = 2\pi\sqrt{LC}$. Consequently,

$$t = \frac{T}{4} = \frac{2\pi\sqrt{LC}}{4} = \frac{2\pi\sqrt{(0.050\text{ H})(4.0\times 10^{-6}\text{ F})}}{4} = 7.0\times 10^{-4}\text{ s}.$$

24. The charge q after N cycles is obtained by substituting $t = NT = 2\pi N/\omega'$ into Eq. 31-25:

$$\begin{aligned} q &= Qe^{-Rt/2L} \cos(\omega't + \phi) = Qe^{-RNT/2L} \cos[\omega'(2\pi N/\omega') + \phi] \\ &= Qe^{-RN(2\pi\sqrt{L/C})/2L} \cos(2\pi N + \phi) \\ &= Qe^{-N\pi R\sqrt{C/L}} \cos\phi. \end{aligned}$$

We note that the initial charge (setting $N = 0$ in the above expression) is $q_0 = Q \cos \phi$, where $q_0 = 6.2\text{ }\mu\text{C}$ is given (with 3 significant figures understood). Consequently, we write the above result as $q_N = q_0 \exp(-N\pi R\sqrt{C/L})$.

(a) For $N = 5$, $q_5 = (6.2\text{ }\mu\text{C}) \exp(-5\pi(7.2\Omega)\sqrt{0.0000032\text{ F}/12\text{ H}}) = 5.85\text{ }\mu\text{C}.$

(b) For $N = 10$, $q_{10} = (6.2\text{ }\mu\text{C}) \exp(-10\pi(7.2\Omega)\sqrt{0.0000032\text{ F}/12\text{ H}}) = 5.52\text{ }\mu\text{C}.$

(c) For $N = 100$, $q_{100} = (6.2\text{ }\mu\text{C}) \exp(-100\pi(7.2\Omega)\sqrt{0.0000032\text{ F}/12\text{ H}}) = 1.93\text{ }\mu\text{C}.$

28. (a) We use $I = \mathcal{E}/X_C = \omega_d C \mathcal{E}$:

$$I = \omega_d C \mathcal{E}_m = 2\pi f_d C \mathcal{E}_m = 2\pi(1.00\times 10^3\text{ Hz})(1.50\times 10^{-6}\text{ F})(30.0\text{ V}) = 0.283\text{ A}.$$

(b) $I = 2\pi(8.00\times 10^3\text{ Hz})(1.50\times 10^{-6}\text{ F})(30.0\text{ V}) = 2.26\text{ A}.$

29. (a) The current amplitude I is given by $I = V_L/X_L$, where $X_L = \omega_d L = 2\pi f_d L$. Since the circuit contains only the inductor and a sinusoidal generator, $V_L = \mathcal{E}_m$. Therefore,

$$I = \frac{V_L}{X_L} = \frac{\mathcal{E}_m}{2\pi f_d L} = \frac{30.0\text{ V}}{2\pi(1.00\times 10^3\text{ Hz})(50.0\times 10^{-3}\text{ H})} = 0.0955\text{ A} = 95.5\text{ mA}.$$

(b) The frequency is now eight times larger than in part (a), so the inductive reactance X_L is eight times larger and the current is one-eighth as much. The current is now

$$I = (0.0955 \text{ A})/8 = 0.0119 \text{ A} = 11.9 \text{ mA}.$$

30. (a) The current through the resistor is

$$I = \frac{\mathcal{E}_m}{R} = \frac{30.0 \text{ V}}{50.0 \Omega} = 0.600 \text{ A}.$$

(b) Regardless of the frequency of the generator, the current is the same, $I = 0.600 \text{ A}$.

62. We use Eq. 31-79 to find

$$V_s = V_p \left(\frac{N_s}{N_p} \right) = (100 \text{ V}) \left(\frac{500}{50} \right) = 1.00 \times 10^3 \text{ V}.$$

63. (a) The stepped-down voltage is

$$V_s = V_p \left(\frac{N_s}{N_p} \right) = (120 \text{ V}) \left(\frac{10}{500} \right) = 2.4 \text{ V}.$$

(b) By Ohm's law, the current in the secondary is $I_s = \frac{V_s}{R_s} = \frac{2.4 \text{ V}}{15 \Omega} = 0.16 \text{ A}$.

We find the primary current from Eq. 31-80:

$$I_p = I_s \left(\frac{N_s}{N_p} \right) = (0.16 \text{ A}) \left(\frac{10}{500} \right) = 3.2 \times 10^{-3} \text{ A}.$$

(c) As shown above, the current in the secondary is $I_s = 0.16 \text{ A}$.